

assignment2

February 5, 2024

- for the following circuit, the correct logic values for the entries $X2$ and $Y2$ in the truth table are (PH2019,36)

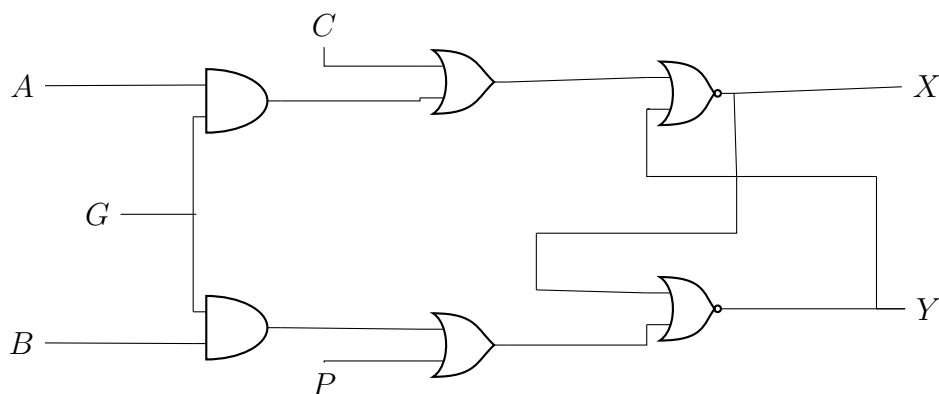


Figure 1: logic diagram

G	A	B	P	C	X	Y
1	0	1	0	0	0	1
0	0	0	1	0	X2	Y2
1	0	0	0	1	0	1

- 1 and 0
- 0 and 0
- 0 and 1
- 1 and 1